

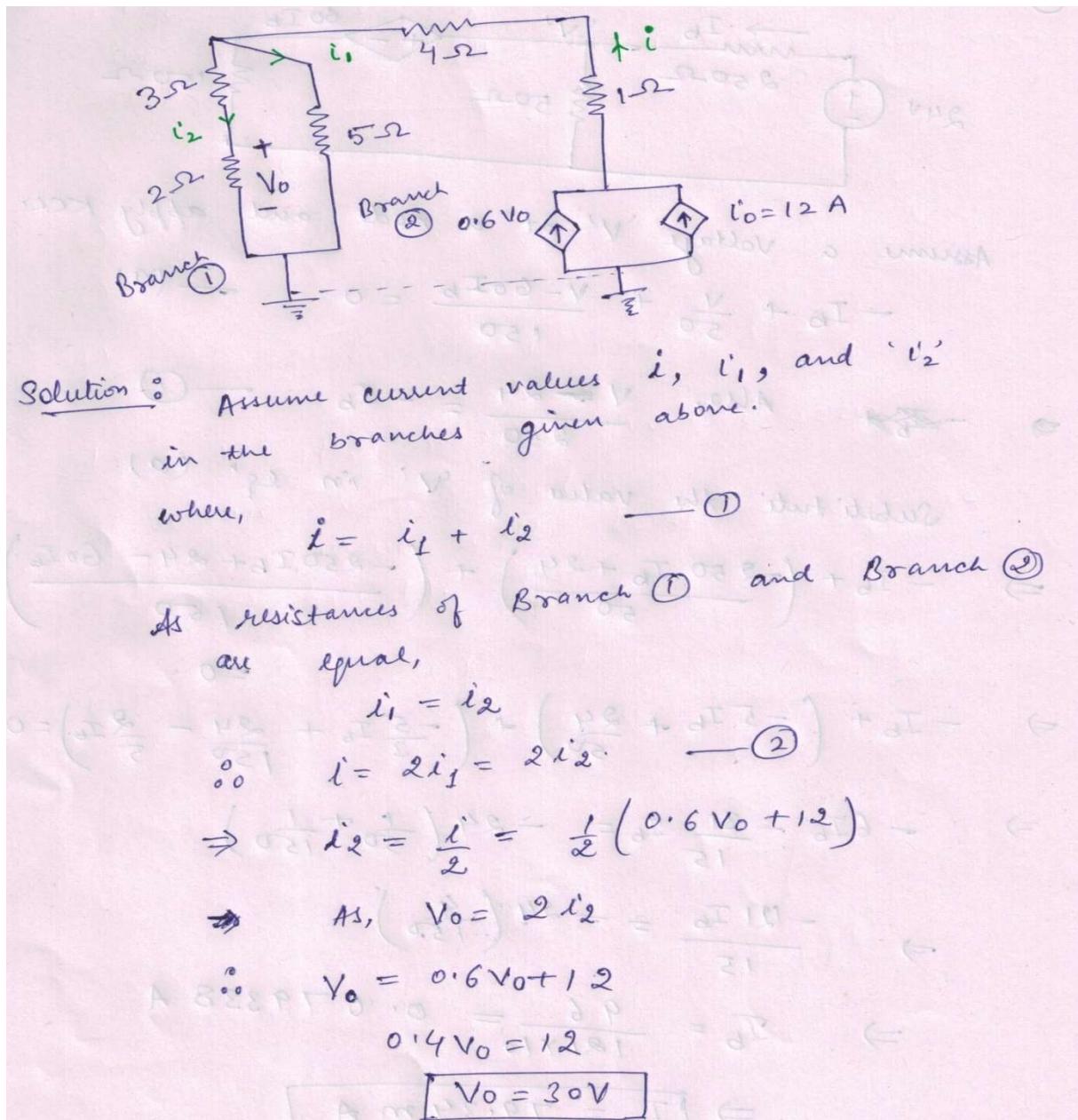


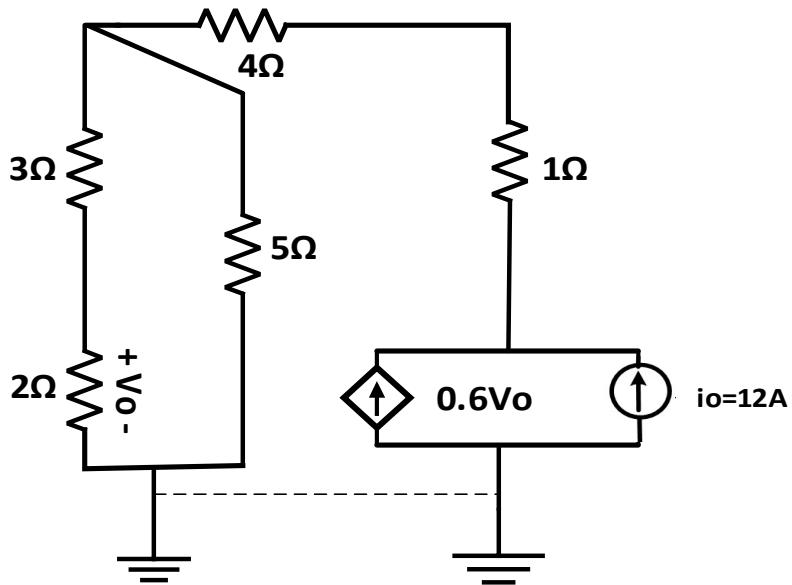1. Calculate the value of 'Vo' in the circuit shown below.



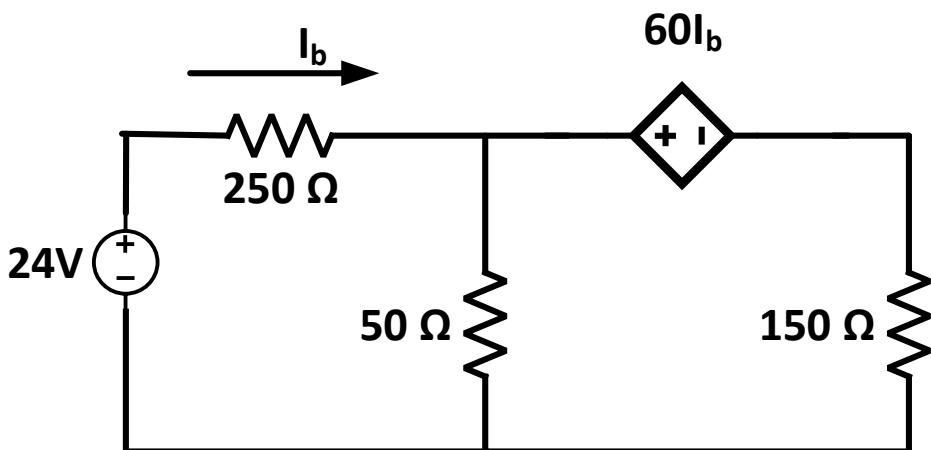2. Calculate the current 'I<sub>b</sub>' in the circuit shown below:



Assume a voltage 'V' at a node and apply KCL

$$-I_b + \frac{V}{50} + \frac{V - 60I_b}{150} = 0 \quad \text{(a)}$$

~~Also,~~  $\frac{V - 24}{250} = -I_b \quad \text{(1)}$

Substitute the value of 'V' in eqn (a).

$$\Rightarrow -I_b + \left( \frac{-250I_b + 24}{50} \right) + \left( \frac{-250I_b + 24 - 60I_b}{150} \right) = 0$$

$$\Rightarrow -I_b + \left( -\frac{5I_b}{3} + \frac{24}{50} \right) + \left( -\frac{5I_b}{3} + \frac{24}{150} - \frac{2I_b}{5} \right) = 0$$



$$\Rightarrow -6I_b - \frac{31}{15}I_b = -24 \left( \frac{1}{50} + \frac{1}{150} \right)$$

$$\Rightarrow \frac{-121I_b}{15} = -24 \left( \frac{4}{150} \right)$$

$$\Rightarrow I_b = \frac{96}{121 \times 10} = 0.079338 A$$

$$\Rightarrow I_b = 79.34 \text{ mA}$$

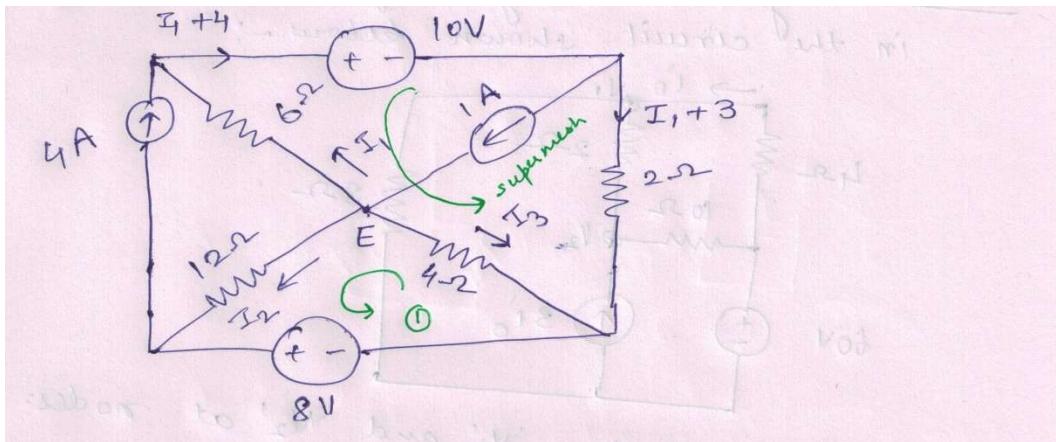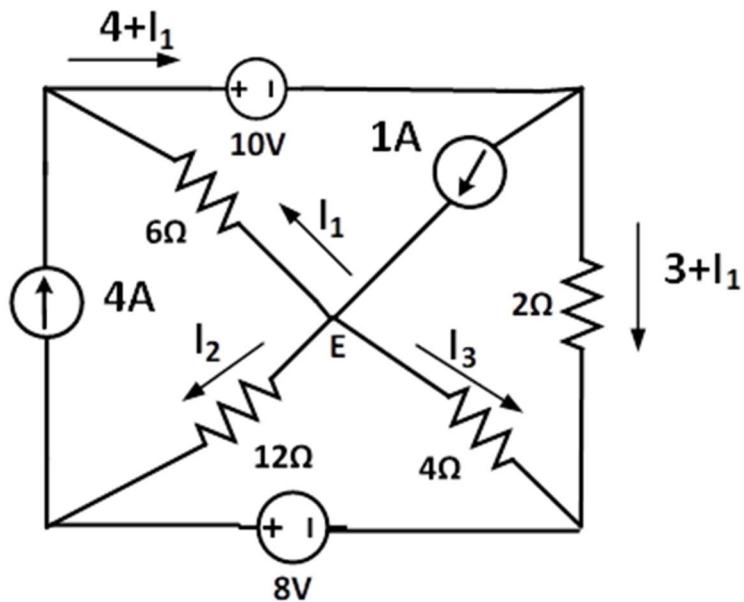3. In the circuit, find current  $I_1$ ,  $I_2$ , and  $I_3$ :



Here,

$$I_1 + I_2 + I_3 = 1 \quad \text{--- (1)}$$

KVL in Loop - (1)

$$12I_2 + 8 - 4I_3 = 0 \quad \text{--- (2)}$$

KVL in supermesh

$$-10 - 6I_1 + 4I_3 - 2(I_1 + 3) = 0$$

$$\Rightarrow -8I_1 + 4I_3 - 16 = 0$$



$$\Rightarrow -2I_1 + I_3 = 4 \quad \text{--- (3)}$$

Solving eqns (1), (2), and (3)

we get,

$I_1 = -1A$
$I_2 = 0$
$I_3 = 2A$

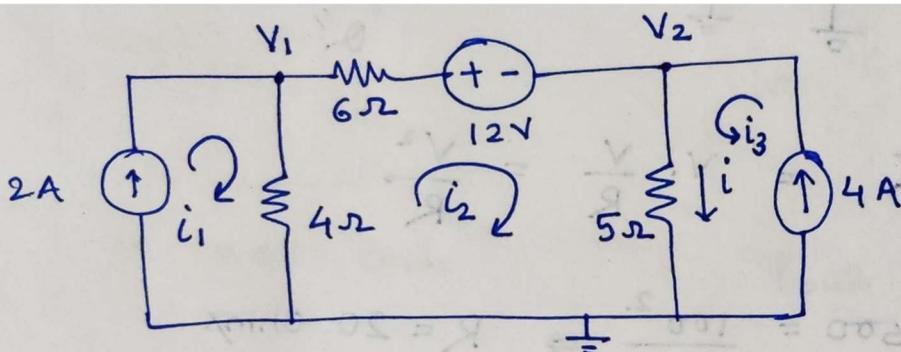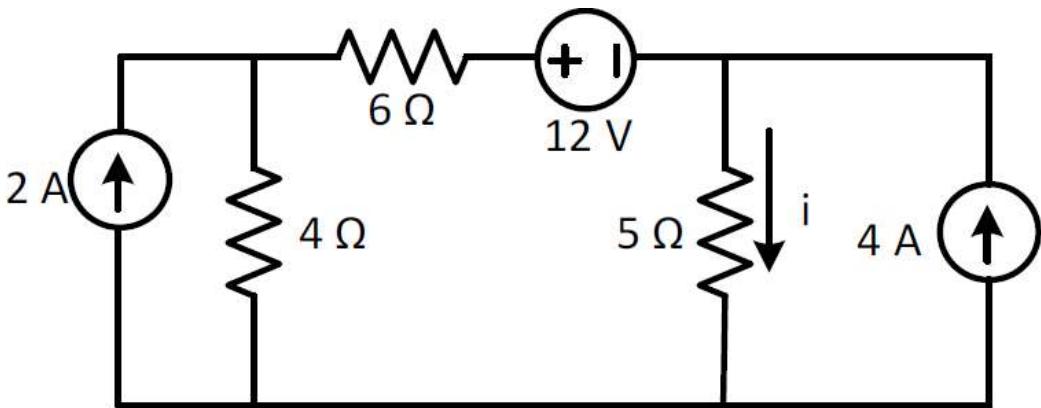4. Find the current  $i$  of the following circuit.



$$\text{Here, } i_1 = 2 \text{ A}, \quad i_3 = 4 \text{ A}, \quad i = i_2 + i_3$$

$$\text{also, } V_1 = 4(i_1 - i_2) = 4(2 - i_2)$$

$$V_2 = 5 \times i = 5 \times (i_2 + i_3) = 5 \times (i_2 + 4)$$

$$V_1 - V_2 = 4(2 - i_2) - 5(i_2 + 4)$$

$$V_1 - V_2 = 8 - 4i_2 - 5i_2 - 20$$

$$V_1 - V_2 = -9i_2 - 12 \quad \text{--- (1)}$$


$$\text{also, } V_1 - V_2 = 6i_2 + 12 \quad \text{--- (2)}$$

$$-9i_2 - 12 = 6i_2 + 12$$

$$i_2 = -\frac{24}{15} = -\frac{8}{5} = -1.6 \text{ Amp}$$

$$\therefore i = i_2 + i_3 = -1.6 + 4 = \underline{\underline{2.4 \text{ Amp}}}$$

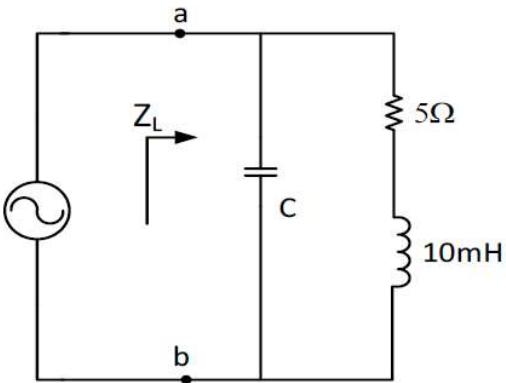5. A source ( $\omega = 314 \text{ rad/s}$ ) is connected to a load  $Z_L$  as shown in Figure. Find the value of the capacitance for the load  $Z_L$  to be completely resistive.



$$Z_L = \frac{-j}{\omega C} \parallel (5 + j\omega L)$$

$$Z_L = \frac{(5 + j\omega L)(-\frac{j}{\omega C})}{5 + j\omega L - \frac{j}{\omega C}}$$

$$Z_L = \frac{\frac{L}{C} - j \frac{5}{\omega C}}{5 + j(\omega L - \frac{1}{\omega C})} \times \frac{5 - j(\omega L - \frac{1}{\omega C})}{5 - j(\omega L - \frac{1}{\omega C})}$$


$$Z_L = \frac{\left(\frac{L}{C} - j \frac{5}{\omega C}\right)\left(5 - j(\omega L - \frac{1}{\omega C})\right)}{5^2 + \left(\omega L + \frac{1}{\omega C}\right)^2}$$

Comparing Imaginary part of  $Z_L$  to zero,

$$C = 287 \mu F$$

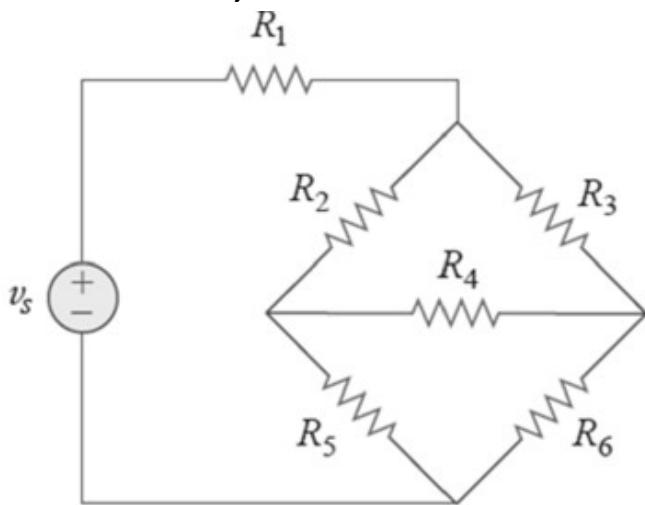6. Find the current flowing through resistor  $R_1$ . Given that –

$V_s = 100 \text{ Volts}$ ,  $R_1 = R_2 = R_3 = R_4 = 5 \Omega$ ,  $R_5 = 1 \Omega$ ,  $R_6 = 2 \Omega$ .



(Use Star – Delta Transformation)

